

Impedance Matching Using Cascaded Boost-Buck Converter For High Efficiency in WPT

Presented by,

Chinchu Joshy

Register No:ADR17EE015

EEE

College Of Engineering Adoor

CONTENTS


- Introduction
- Topologies of different converters
- Block diagram
- Circuit Diagram
- Working of Proposed System
- Graph
- Result
- Conclusion
- References

INTRODUCTION


- Wireless power transmission is one of the most promising technology for the future
- We have various wireless power transfer technologies like inductive coupling , magnetic resonance coupling , microwave etc.
- The main architecture of WPT consist of power source , converter , amplifier , antennas , rectifying circuits and power regulating circuit.
- One of the main challenge of WPT is the design of the system to transfer power efficiently
- This paper introduce a best converter topology for impedance matching for efficient wireless power transfer

WAVEFORMS OF DC-DC CONVERTERS IN CCM AND DCM

CCM

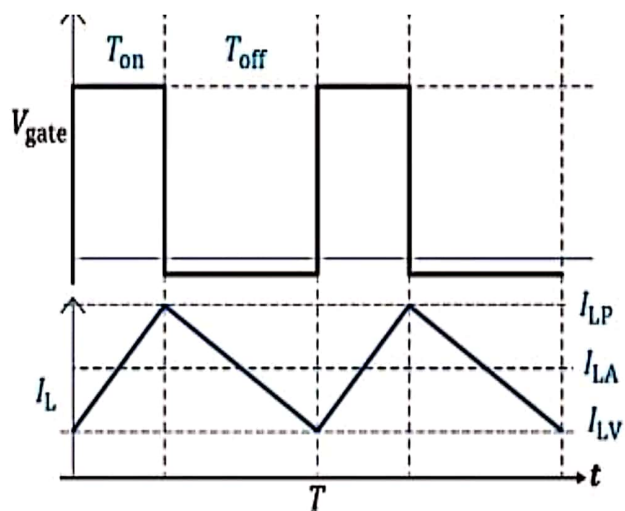


DCM

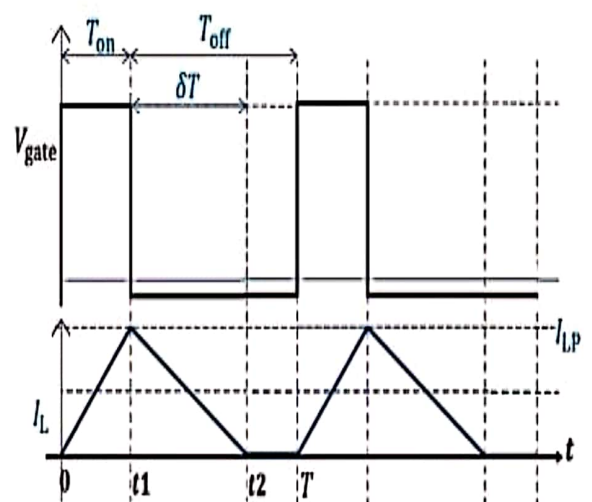

TOPOLOGIES OF DIFFERENT CONVERTERS

Buck converter (DCM)

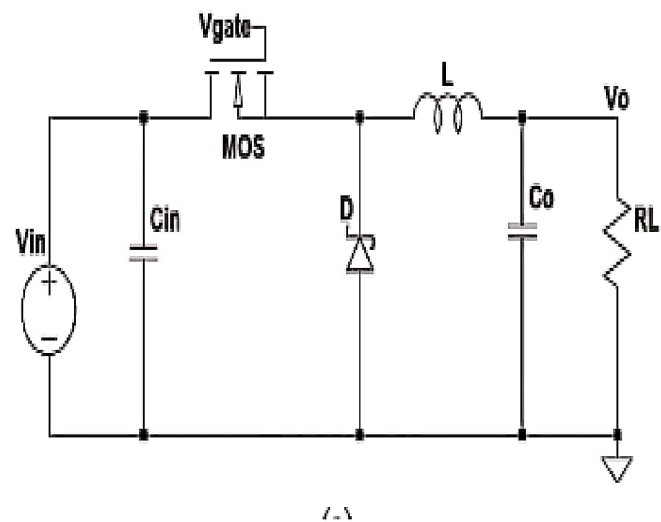
- Output current $I_0 = \frac{1}{2}(D+\delta)I_{Lp}$.
- $R_{in} = (2Lf_{sw}/D^2) \frac{1}{1-V_0/V_{in}}$
- Output voltage $V_0 = \frac{V_{in}^2}{\frac{2LI_0}{D^2} + V_{in}}$



TOPOLOGIES OF DIFFERENT CONVERTERS (cont..)

Boost converter (CCM)

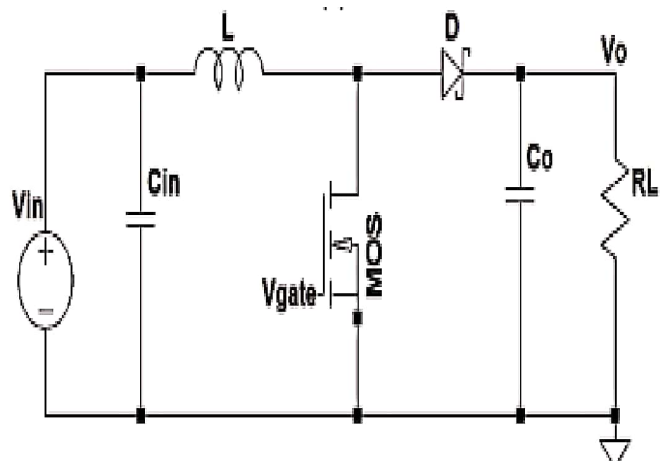
- The inductor current is increasing nearly to the peak value I_L .
- $V_o = (1/1-D)V_{in}$
- $R_{in} = (1-D)^2 R_L$
- In boost converter $R_{in} < R_L$



TOPOLOGIES OF DIFFERENT CONVERTERS (cont..)

Buck-Boost converter (DCM)

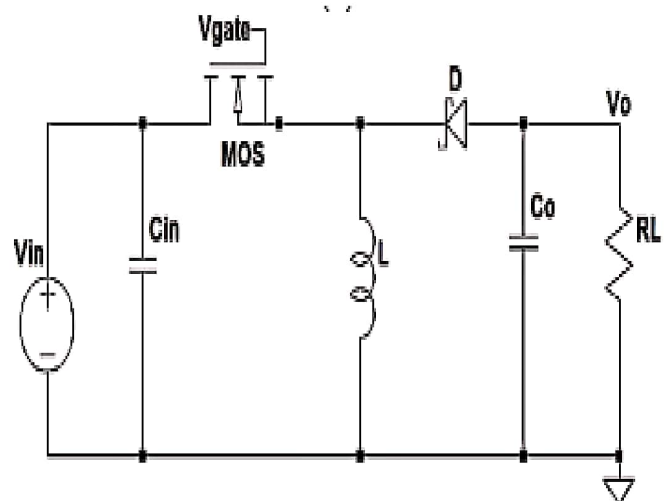
- $I_0 = \delta (I_{LP} / 2)$
- $P_0 = \frac{D^2 T V_{in}^2}{2LI_0}$
- $R_{in} = \frac{2Lf_{sw}}{D^2}$
- f_{sw} is the frequency of the V_{gate}
- R_{in} is independent of the input Voltage and load resistance R_L




TOPOLOGIES OF DIFFERENT CONVERTERS (cont..)

Cascaded Boost-Buck converter

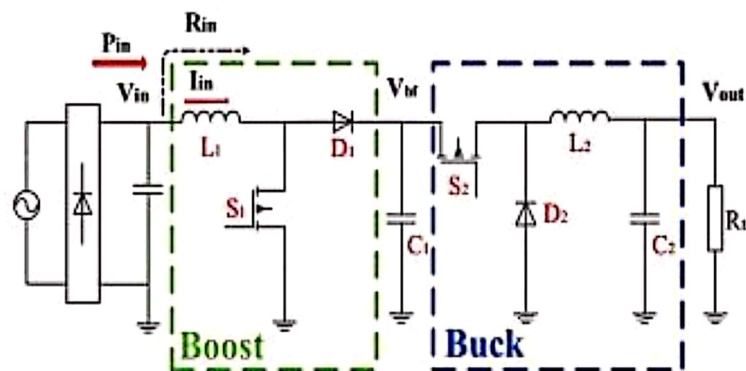- It uses the combination of boost and buck converter
- Compared to one switch topologies the boost-buck two switch topologies provides more flexibility.
- Hence it is considered as the best converter topology for the impedance matching in WPT.
- It has two control modes , fixed load mode and variable load mode.



BLOCK DIAGRAM OF WPT

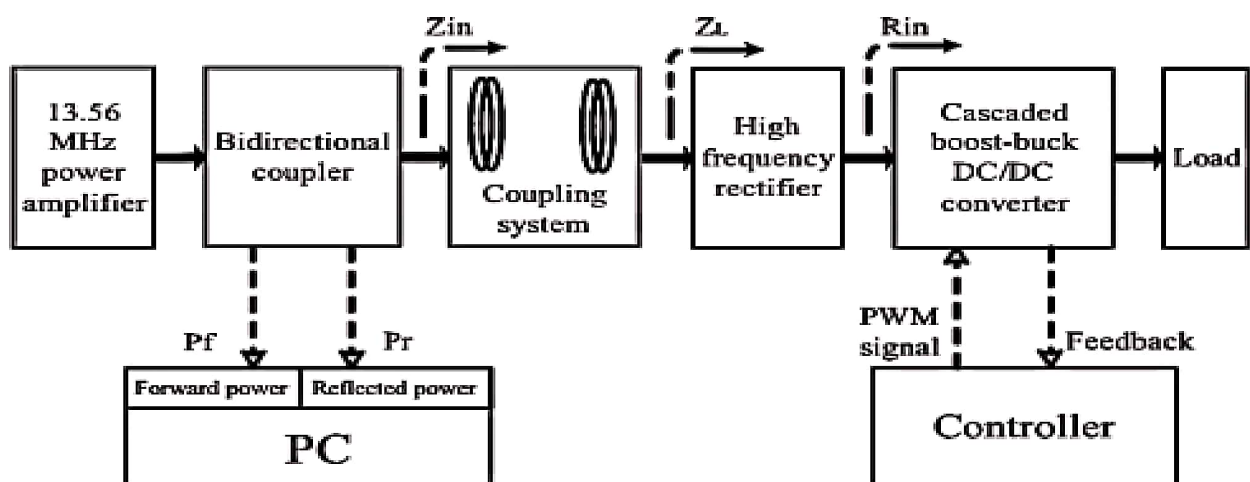

WORKING OF THE PROPOSED SYSTEM


- Here we consider a wireless power transmission system in which the resonant coupling operating at 13.56MHz.
- Electrical energy is fed from suitable energy source is tranfered to a coupling system consisting of a transmitter coil and receiving coil.It tranfer electrical energy by magnetic resonance.
- In order to achieve a high efficiency in WPT system each element should have proper impedance matching
- Optimal load impedance at the receiving coil is designed to minimize power loss

WORKING OF THE PROPOSED SYSTEM(cont..)

- Then the AC signal is converted back to DC using suitable rectifying circuit
- Here we use cascaded Boost-Buck converter to control the equivalent resistance
- In fixed load mode $V_0 = D_2 V_{bf}$
- Assuming constant power loss $V_{in}^2 / R_{in} = V_{out}^2 / R_L$
- $R_{in} = \frac{(1-D_1)^2 R_L}{D_2^2}$
- So resistive load can be matched by using the constant duty cycle control

WORKING OF THE PROPOSED SYSTEM(cont..)

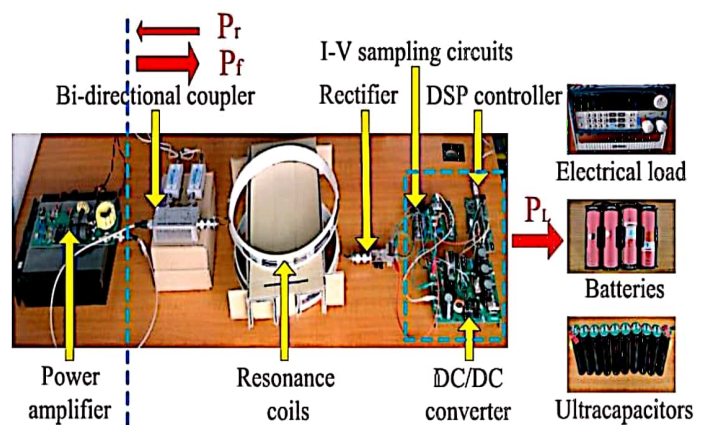- In variable load mode for the dynamic control of the R_{in} the duty cycle D_1 is controlled to maintain a fixed R_{in} .
- D_2 is controlled to provide a $V_{bf} = kV_{in}$
- Where $R_{in} = \frac{V_{bf}^2 (1-D)^2}{P_{in}}$





WORKING OF THE PROPOSED SYSTEM(cont..)

- By proper impedance matching we can transfer maximum power hence we can improve the efficiency in WPT
- In practical case the load may not be resistive because the electrical impedance changes during the charging time
- The proposed cascade boost-buck converter can automatically adjust the duty ratio for optimal system efficiency



GRAPH

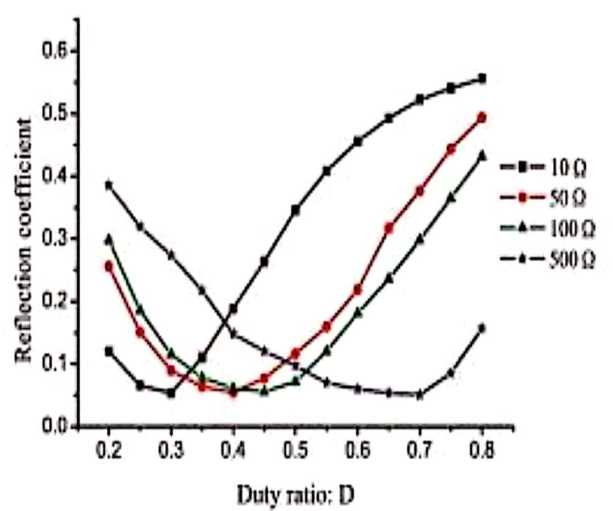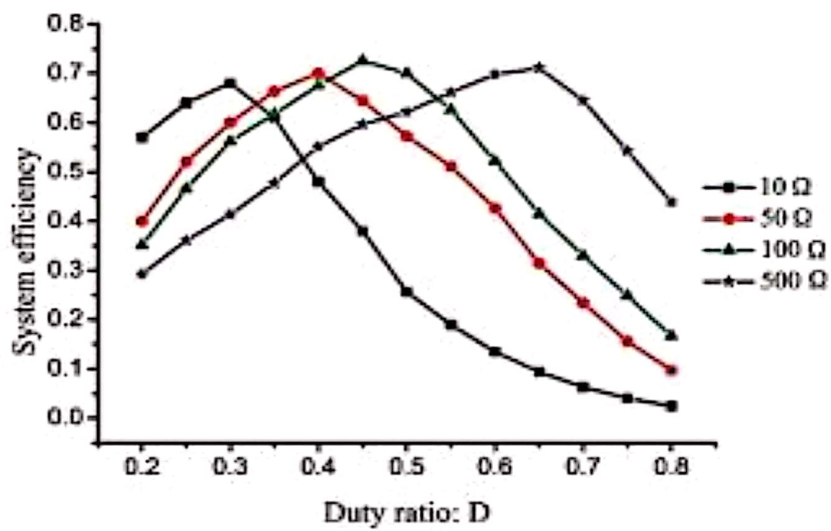System efficiency and reflection coefficient with various duty cycle



GRAPH

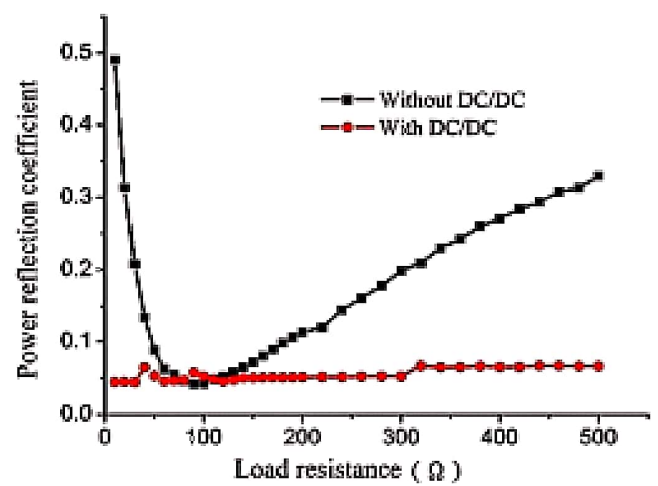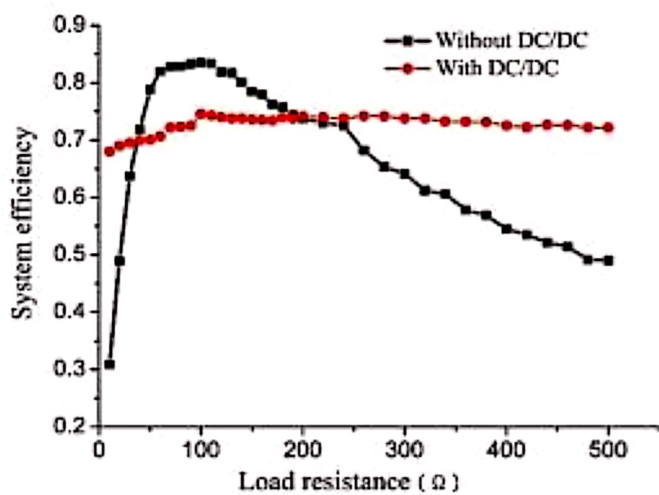System efficiency and reflection coefficient improvement using the cascaded boost-buck DC-DC converter



RESULT

- The best converter topology for the impedance matching in WPT is the cascaded boost-buck converter
- It can help in optimal impedance matching and helps in isolating dynamic load from the system

CONCLUSION

- A new cascaded Boost-Buck converter for impedance matching in WPT system is presented
- This paper explains the working and advantages of boost-buck converter
- This method is universal and applicable for all wireless power transfer technologies

REFERENCES

- Impedance Matching in Wireless Power Transfer(Yong Huang,member IEEE,Naoki Shinohara, member IEEE and Tomohiko Mitani,member IEEE)
- A Cascaded Boost-Buck Converter for High Efficiency Wireless Power Transfer Systems(Minfan Fu,student member IEEE,Chengbin Ma,member IEEE,Xienen ZHU,member IEEE)
- Theoretical Analysis on DC-DC Converter for Impedance Matching of a Rectifying Circuit in Wireless Power Transfer(2015 IEEE International Symposium on Radio frequency integration Technology)

THANK YOU...